## Indian Institute of Information Technology Vadodara International Campus Diu



Practical Workbook

Name : Shreyas Ladhe Roll No. : 202211081

Branch. : Computer Science and Engineering

Batch : 2022

Subject : Digital Logic Design

## Certificate

This is certify that **Shreyas Ladhe** of B.tech of semester III .Enrollment Number **202211081** Branch Computer Science and Engineering (CSE) has been found satisfactory in the continuous internal evaluation of laboratory, practical and term work in the subject EC261 for the academic year 2022-23.

Signature

# List of Experiments

Lab No.	Lab Name	Date	
1	Familiarity with Logic Gates	22 - 09 - 2023	

### 1 Lab-1: Gradient, Divergence and Curl

#### 1.1 Aim

Basic familiarity with logic gate. Verify the truth table of given 74 series IC.


- AND
- NAND
- $\bullet$  NOT
- NOR
- $\bullet \ \mathrm{OR}$
- $\bullet$  XOR

#### 1.2 Apparatus

Sr No.	Components	Quantity
1	Digital Trainer Kit	1
2	NAND (7400)	1
3	NOR (7402)	1
4	NOT (7404)	1
5	AND (7408)	1
6	OR (7432)	1
7	XOR (7486)	1
8	Connecting Wires	As Required
9	Bread board	1
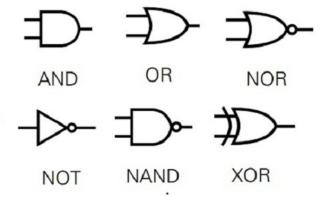
#### 1.3 Theory

Here is a small rundown about the logic gates we are working on:



#### 1.4 Observation

We verified the following truth tables for the logic gates: The sequence is as follows (left to right):-

- AND
- $\bullet$  OR
- $\bullet$  NOT
- NAND
- NOR
- XOR

Inpu	ts	Output
Α	В	AB
0	0	0
0	1	0
1	0	0
1	1	1

Inpu	ıts	Output
Α	В	A + B
0	0	0
0	1	1
1	0	1
1	1	1

Inputs	Output
Α	В
0	1
1	0

Inputs		Output
Α	В	AB
0	0	1
0	1	1
1	0	1
1	1	0

Inpu	ts	Output
Α	В	A+B
0	0	1
0	1	0
1	0	0
1	1	0

Inpu	its	Output
Α	В	A (+) B
0	0	0
0	1	1
1	0	1
1	1	0

### 1.5 Conclusion

Learned about different IC and hands on experience on working with logic gates. Verified the working of all the logic gates.