Subject: Digital Logic Design Lab   Branch: CSE
Course Code:EC261   Semester: III

3 Perform the following

(a) 2-bit adder and subtractor using basic gate or universal gate

(b) Binary to gray code converter

(c) Binary to BCD converter